

# Implementation of Boolean Logic in Arduino using IC 7474

Sai Harshith kalithkar  
harshith.work@gmail.com  
FWC22118

IIT Hyderabad-Future Wireless Communication Assignment

February 2023


## Contents

<b>1 Problem</b>	<b>1</b>
<b>2 Introduction</b>	<b>2</b>
<b>3 Components</b>	<b>2</b>
<b>4 Hardware</b>	<b>3</b>
<b>5 Software</b>	<b>3</b>

## 1 Problem

(GATE EC-2022)

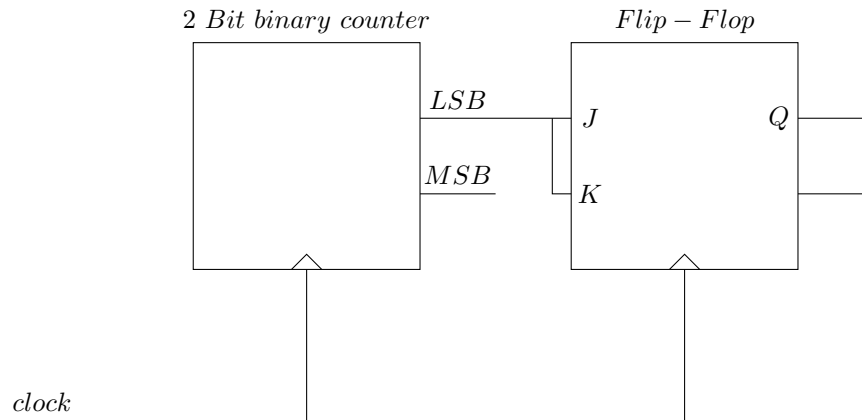Q.43. For the circuit shown, the clock frequency is  $f_0$  and the duty cycle is 25%. For the signal at the  $Q$  output of the Flip-Flop,



1. frequency of  $\frac{f_0}{4}$  and duty cycle is 50%
2. frequency of  $\frac{f_0}{4}$  and duty cycle is 25%
3. frequency of  $\frac{f_0}{2}$  and duty cycle is 50%
4. frequency of  $f_0$  and duty cycle is 25%

## 2 Introduction

The Aim is to implement the above circuit in Arduino using IC 7474. IC 7474 is a dual positive-edge-triggered D-type flip-flop, which means it has two separate flip-flop that are triggered by the rising edge of a clock signal. A 2-bit binary counter can be implemented using 2 D Flip-flops similarly a JK Flip-flop can be implemented using one D Flip-flop. Thus we will use two IC 7474 to implement the whole circuit.


The LSB output of the 2-bit binary counter is given to J and K inputs of the JK Flip-flop which then gives the final Q output of the circuit. Since the inputs given to J and K are same it acts as T Flip-flop.

## 3 Components

1. Arduino UNO
2. IC 7474 - 2 units
3. Breadboard
4. Jumper Wires (M-M)
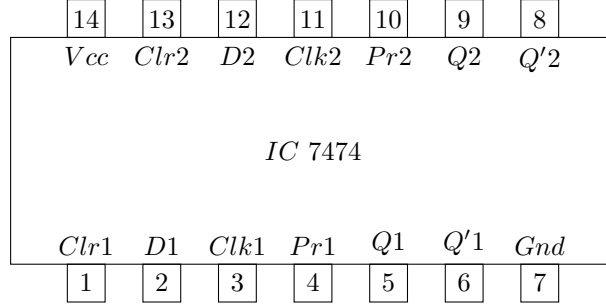
## 4 Hardware

The IC 7474 is a type of flip-flop integrated circuit that is commonly used in digital electronics applications. It is a dual positive-edge-triggered by the rising edge of a clock signal. Below is the pin diagram of IC 7474.



The connections between Arduino UNO and two IC 7474 is given in below Table

	INPUT	OUTPUT			CLOCK		$V_{cc}$	GND
ARDUINO	D6	D3	D4	D5	D2		5V	GND
7447		5			3	11	14	7
7474	5		9	2	3		14	7

Table 1: Connections

The truth table for the circuit is given in below table

counter	MSB	LSB	J	K	$Q(t)$	$Q(t+1)$
0	0	0	0	0	0	0
1	0	1	1	1	0	1
2	1	0	0	0	1	1
3	1	1	1	1	1	0

Table 2: Truth Table

## 5 Software

The Arduino code for the given circuit using IC 7474 is

---

```

#include<Arduino.h>

int clockPin = 2; //clock input pin
int q1Pin = 3; //Q output of flip-flop 1 of first IC 7474
int q2Pin = 4; //Q output of flip-flop 2 of first IC 7474
int dPin = 5; //D input of flip-flop of second IC 7474
int qPin = 6; //Q output of flip-flop of second IC 7474

void setup(){
    pinMode(qPin, INPUT);
    pinMode(clockPin, OUTPUT);
    pinMode(q1Pin, OUTPUT);
    pinMode(q2Pin, OUTPUT);
    pinMode(dPin, OUTPUT);
    pinMode(13, OUTPUT);

    //Initialize outputs
    digitalWrite(clockPin, LOW);
    digitalWrite(q1Pin, LOW);
    digitalWrite(q2Pin, LOW);
    digitalWrite(qPin, LOW);
}

void jk_flipflop(int q1){ //code for JK flip-flop with LSB of 2 bit
    counter as input to both J and K
    int q = digitalRead(qPin);
    int d = q1^q;
    digitalWrite(dPin, d);
    digitalWrite(13, q);
}

void loop(){
    digitalWrite(clockPin, LOW);
    delay(10);
    digitalWrite(clockPin, HIGH);

    int q1=digitalRead(q1Pin);
    int q2=digitalRead(q2Pin);

    q1=!q1;
    if(q1==HIGH) q2=!q2;

    digitalWrite(q1Pin, q1);
    digitalWrite(q2Pin, q2);
    jk_flipflop(q1);
    delay(1000);
}

```

---